

## Experiment 1: C-V Measurements

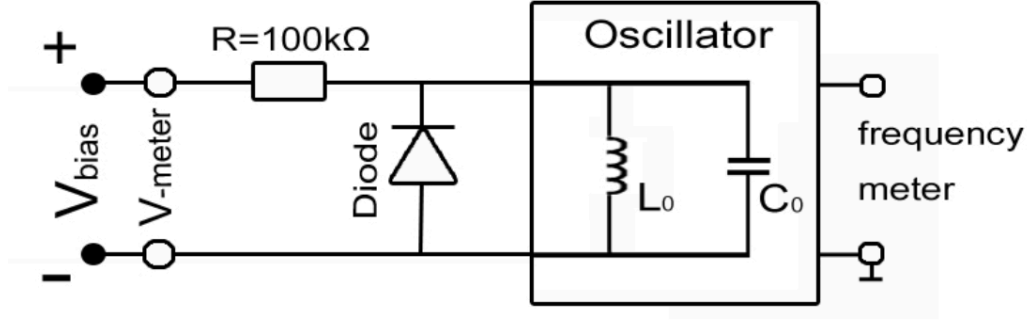


Figure 1: Circuit Diagram for CV Measurements

The circuits shown in Figure 1 is used to conduct the CV Measurements.

The open-loop frequency of the oscillator  $f_0 = 1629.9 \pm 0.05\text{kHz}$ .

The "10 pF" capacitor  $C_{10} = 10.48 \pm 0.005\text{pF}$ .

With  $C_{10}$  connected, the frequency  $f_{10} = 1467.4 \pm 0.05\text{kHz}$ .

From theories of oscillators, the circuit capacitance  $C_0 = \frac{C_{10}}{\left(\frac{f_0^2}{f_{10}^2}\right) - 1} = 44.84 \pm 0.054\text{pF}$ . The error  $\Delta C_0$

is found by:  $\Delta C_0 \approx \left|\frac{\partial C_0}{\partial C_{10}}\right| \Delta C_{10} + \left|\frac{\partial C_0}{\partial f_0}\right| \Delta f_0 + \left|\frac{\partial C_0}{\partial f_{10}}\right| \Delta f_{10}$ .

In this experiment, the total capacitance  $C_r$  is consisted of the stray capacitance  $C_s$ , and capacitance of the depletion region  $C_{diode}$ :  $C_r = C_s + C_{diode}$ .

Where  $C_s$  is constant and  $C_{diode} = A_c \left(\frac{\epsilon_s e N_d}{2(V_0 - V_{rev})}\right)^{1/2}$ ,  $V_0 = 0.5\text{V}$  is the built-in voltage.

The bias voltage  $V_{rev}$  is varied in a range and corresponding  $C_r$  is found from  $C_r = C_0 \left[\left(\frac{f_0}{f_r}\right)^2 - 1\right]$ , where  $f_r$  is the frequency measured on the frequency meter.

The data table is shown in Figure 9 in appendix.

To extrapolate  $C_s$  and  $N_D$  from the data, a scatter plot and a linear fit are applied, where  $C_r$  is plotted against  $(V_0 - V_{ref})^{-1/2}$ .

Rearrangements gives:  $C_r = C_s + [A_d \left(\frac{\epsilon_s e N_D}{2}\right)^{1/2}] \cdot (V_0 - V_{ref})^{-1/2}$ .

For the linear fit  $y = kx + b$ ,  $C_s = b$  and  $N_D = \frac{2}{\epsilon_s e} \left(\frac{k}{A_c}\right)^2$ .

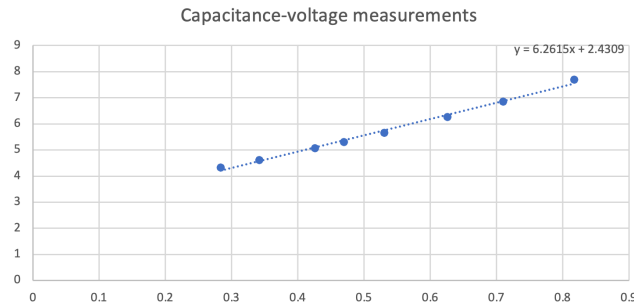


Figure 2: Linear Fit of the CV Measurements

With  $k = 6.2615$ ,  $b = 2.4309$ ,  $C_s = 2.4309 pF$ ,  $N_D = 8.2 \times 10^{26} m^{-3}$ .

## Experiment 2: I-V Measurements

### Reverse Bias

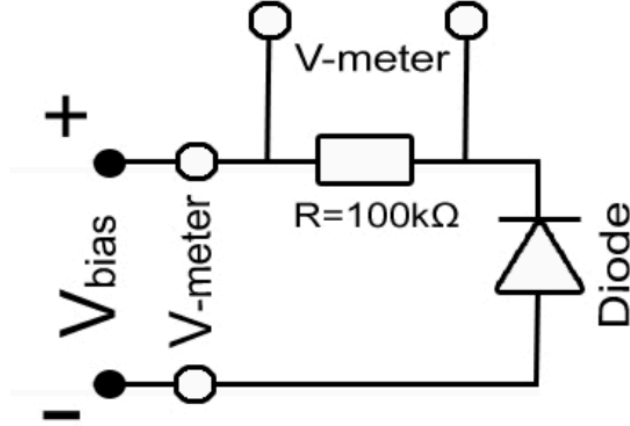


Figure 3: Circuit Diagram of Measuring Reverse Saturation Current

Figure 3 shows the circuits diagram for measuring reverse saturation current under reverse bias.

The reverse current  $I_{rev}$  is related to reverse saturation current  $I_s$  and leak resistance  $R_{leak}$  by:

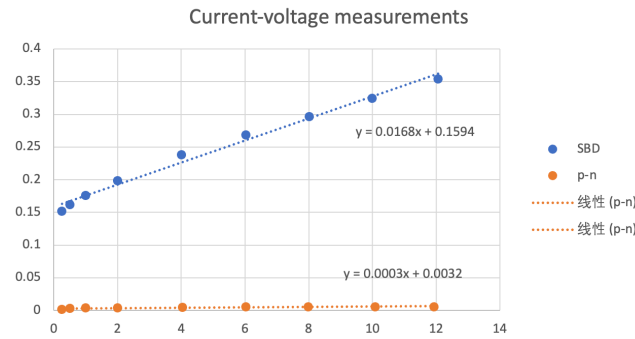
$$I_{rev} = I_s \left[ \exp \frac{eV_{rev}}{\eta k T} - 1 \right] + \frac{V_{rev}}{R_{leak}}$$


Figure 4: Linear Fit for Current - Voltage Measurements

Figure 4 shows a linear fit of measured values of  $I_{rev} - V_{rev}$ .

The reverse saturation current can be estimated by the intercept as  $I_{rev} \approx -I_s$  when  $V_{rev} = 0$ .  $I_s \approx 0.1594 \mu A$ .

The leak resistance can be estimated by the gradient.  $R_{leak} \approx 59.2 k\Omega$ .

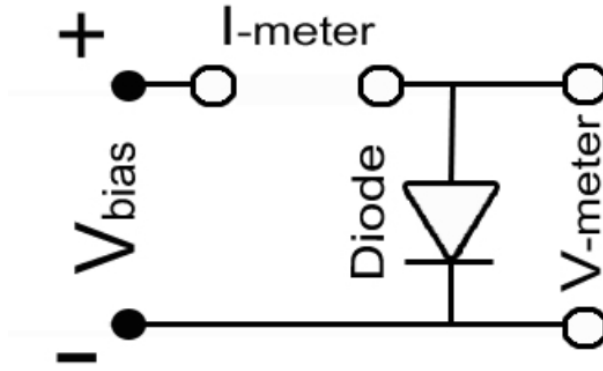


Figure 5: Circuit Diagram of Measuring Forward Current

### Weak Forward Bias

Figure 5 shows the circuits diagram for measuring current under both weak forward bias and strong forward bias.

For a Schottky barrier diode under forward bias,  $I_F = I_s[\exp \frac{eV}{\eta kT} - 1]$ . Rearrangement gives  $V_F = \eta \frac{kT}{e} [\ln(\frac{I_F}{I_s}) + 1]$ .

$V_F$  is plotted against  $(\ln(\frac{I_F}{I_s}) + 1)$ , shown in Figure 6. The gradient equals to  $\eta \frac{kT}{e}$ . Under the lab circumstance,  $\frac{kT}{e} = 25.68mV$ .  $\eta = 1.47$ .

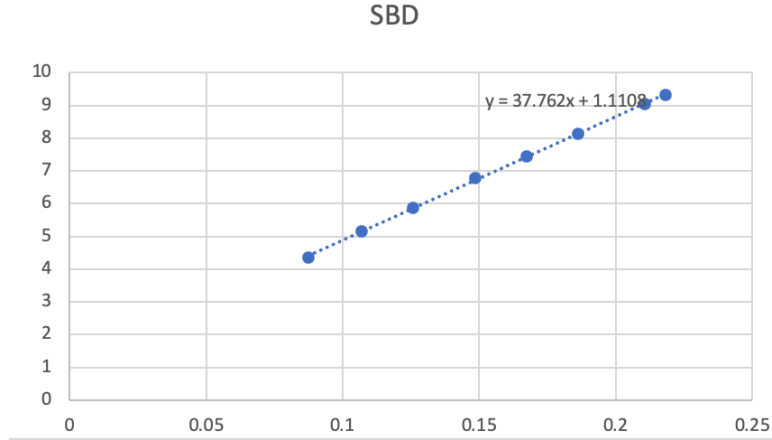


Figure 6: Linear Fit of Forward Voltage and  $\ln(\frac{I_F}{I_s}) + 1$

### Strong Forward Bias

In this section, a same circuit is used as the test in weak forward bias.

From the lab sheet,  $I_F = \frac{1}{r_c}(V_F - \frac{\eta kT}{e} \ln(\frac{I_F}{I_s}))$ .

$r_{cSBD} = 2.5\Omega$ ,  $r_{cpn} = 0.9\Omega$ .

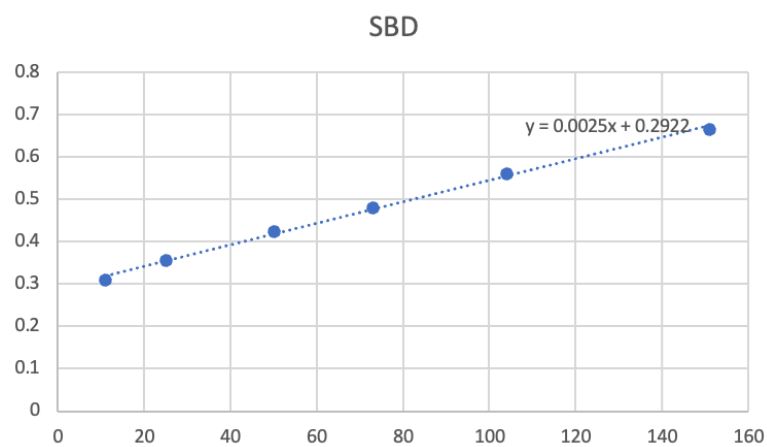


Figure 7: Linear Fit of Forward Voltage and Forward Current

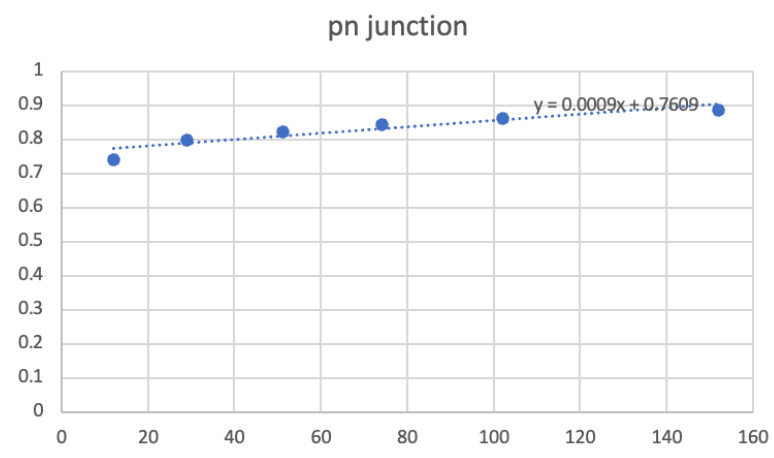


Figure 8: Linear Fit of Forward Voltage and Forward Current

## Data Tables

	10 pf as measured on bridge ↓	Take $V_o = 0.5$ V	Measured Frequency [kHz]	$C_r$ is $C_{SBD}$ corresponding to $f_r$
(+ 10pf) $V_{rev}$ none	$C_{10} = 10.48$ [pF]		$f_{10} = 1467.4$	$C_{10}/[(f_o^2/f_{10}^2)-1] =$ ↓
(+ 0 pf) $V_{rev}$ none			$f_o = 1629.9$	$C_o = 44.83546$
<b>Suggested</b> $V_{rev}$ [V]	<b>Measured</b> $V_{rev}$ [V] ↓	$(V_o - V_{rev})^{-1/2}$ [V <sup>-1/2</sup> ] ↓	$f_r =$ ↓	$C_o [(f_o^2/f_r^2)-1]$ = $C_r$ ↓
-12.0	11.95	0.283410101	1556.63	4.320112786
-8.0	8.05	0.341992784	1551.9	4.620209707
-5.0	5.01	0.426014323	1544.992	5.063452871
-4.0	4.035	0.469581906	1541.339	5.300255742
-3.0	3.048	0.530894461	1535.823	5.661033323
-2.0	2.053	0.625856249	1526.768	6.261781717
-1.5	1.484	0.709952293	1517.936	6.858122776
-1.0	0.998	0.817041457	1505.866	7.690125286

Figure 9: Data Table for CV Measurements

Suggested	Measured	Measured	Measured <i>SBD</i>	Measured	Measured	Measured
$V_{Reverse}$ [V]	$V_{Reverse}$ [V]	SBD (voltage drop at the resistor when SBD connected)	$I_{Rev}$ [μA]	$V_{Reverse}$ [V]	p-n ((voltage drop at the resistor when p-n diode connected)	p-n diode
		$V_{Reverse}$ [mV]			$V_{Reverse}$ [mV]	$I_{Rev}$ [μA]
-0.25	0.2504	15.2	0.152	0.2497	0.2	0.002
-0.50	0.5009	16.2	0.162	0.4962	0.3	0.003
-1.0	1.002	17.6	0.176	0.994	0.4	0.004
-2.0	2.004	19.9	0.199	1.999	0.4	0.004
-4.0	4.004	23.8	0.238	4.042	0.5	0.005
-6.0	6.032	26.9	0.269	6.021	0.6	0.006
-8.0	8.01	29.7	0.297	7.99	0.6	0.006
-10.0	9.99	32.5	0.325	10.09	0.6	0.006
-12.0	12.06	35.4	0.354	11.93	0.6	0.006

Figure 10: Data Table for Reverse Saturation Current

Suggested	Measured	Measured	Measured <i>SBD</i>	Measured	Measured	Measured
$V_{Reverse}$ [V]	$V_{Reverse}$ [V]	SBD (voltage drop at the resistor when SBD connected)	$I_{Rev}$ [ $\mu$ A]	$V_{Reverse}$ [V]	p-n ((voltage drop at the resistor when p-n diode connected))	p-n diode
		$V_{Reverse}$ [mV]			$V_{Reverse}$ [mV]	$I_{Rev}$ [ $\mu$ A]
-0.25	0.2504	15.2	0.152	0.2497	0.2	0.002
-0.50	0.5009	16.2	0.162	0.4962	0.3	0.003
-1.0	1.002	17.6	0.176	0.994	0.4	0.004
-2.0	2.004	19.9	0.199	1.999	0.4	0.004
-4.0	4.004	23.8	0.238	4.042	0.5	0.005
-6.0	6.032	26.9	0.269	6.021	0.6	0.006
-8.0	8.01	29.7	0.297	7.99	0.6	0.006
-10.0	9.99	32.5	0.325	10.09	0.6	0.006
-12.0	12.06	35.4	0.354	11.93	0.6	0.006

Figure 11: Data Table for Weak Forward Bias

	SBD current	SBD forward voltage	p-n current	p-n forward voltage
Suggested	Measured	Measured	Measured	Measured
$I_{forward}$ [mA]	$I_{forward}$ [mA]	$V_{forward}$ [V]	$I_{forward}$ [mA]	$V_{forward}$ [V]
10	11	0.31	12	0.742
25	25	0.3572	29	0.798
50	50	0.424	51	0.823
75	73	0.4822	74	0.844
100	104	0.5616	102	0.863
150	151	0.667	152	0.886

Figure 12: Data Table for Strong Forward Bias